

M.Sc. Sem III

MPHYC - ~~10~~ 12

electronics II

OP-amp

Dr. Shiva Kant Mishra

Dept. of Physics IITJCT


Logarithmic and exponential Amplifiers :-

The electronic Circuits which perform the mathematical operations such as logarithmic and exponential with an amplification are called as Logarithmic amplifier and exponential amplifier respectively.

Logarithmic Amplifier :-

A logarithmic amplifier, or a log amplifier, is an electronic circuit that produces an output that is proportional to the logarithm of the applied input. This section discusses about the op-amp based logarithmic amplifier in detail.

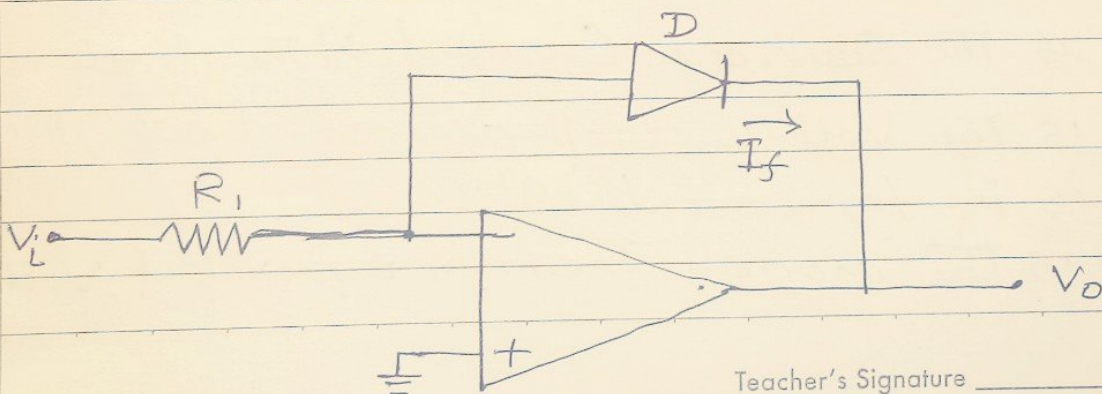An op-amp based logarithmic amplifier produces a voltage at the output, which is proportional to the logarithm of the voltage applied to the resistor connected to its inverting terminal. The circuit diagram of an op-amp based logarithmic amplifier is shown in the following figure.



Teacher's Signature _____

In the above circuit, the non-inverting input terminal of the op-amp is connected to ground. That means zero volts is applied at the non-inverting input terminal of the op-amp.

According to the Virtual Short Concept, the voltage at the inverting input terminal of an op-amp will be equal to the voltage at its non-inverting input terminal. So, the voltage at the inverting input terminal will be zero volts.

The nodal equation at the inverting input terminal's node is —

$$\frac{0 - V_i}{R_1} + I_f = 0$$

$$\Rightarrow I_f = \frac{V_i}{R_1} \quad \text{--- (1)}$$

The following is the equation for current flowing through a diode, when it is in forward bias

$$I_f = I_s e^{\left(\frac{V_f}{nV_T}\right)} \quad \text{--- (2)}$$

Where,

I_s is the Saturation Current of the diode.

V_f is the voltage drop across diode, when it is in forward bias.

V_T is the diode's Thermal equivalent Voltage.

The KVL equation around the feedback loop of the OP-amp will be

$$0 - V_f - V_o = 0$$

$$\Rightarrow V_f = -V_o$$

Substituting the value of V_f in eqn (2), we get,

$$I_f = I_s e^{\left(\frac{-V_o}{nV_T}\right)} \quad \text{--- (3)}$$

observe that the left hand side terms of both eqn (1) and (3) are same. Hence, equate the right hand side term of those two equations as shown below —

$$\frac{V_i}{R_1} = I_s e^{\left(\frac{-V_o}{nV_T}\right)}$$

$$\frac{V_i}{R_1 I_s} = e^{\left(\frac{-V_o}{nV_T}\right)}$$

Applying natural logarithm on both sides, we get —

$$\ln \left(\frac{V_i}{R_1 I_s} \right) = \frac{-V_o}{nV_T}$$

$$V_o = -nV_T \ln \left(\frac{V_i}{R_1 I_s} \right)$$

Note that in the above equⁿ, the parameters n , V_T and I_s are constants. So, the output voltage V_o will be proportional to the natural logarithm of the input voltage V_i , for a fixed value of resistance R_1 .

Therefore, the op-amp based logarithmic amplifier circuit discussed above will produce an output, which is proportional to the natural logarithm of the input voltage

V_T , when $R_1 I_s = 1V$.

Observe that the output voltage V_o has a negative sign, which indicates that there exists a 180° phase difference between the input and the output.
