

M.Sc. Sem III

MPHYC - ~~12~~ 12

electronics II

OP-amp

Dr. Shiva Kant Mishra

Dept. of Physics IIT JCT




## Anti-Logarithmic (Exponential) Amplifier:

An anti-logarithmic amplifier, or an anti-log amplifier, is an electronic circuit that produces an output that is proportional to the anti-logarithm of the applied input. This section discusses about the op-amp based anti-logarithmic amplifier in detail.

An op-amp based anti-logarithmic amplifier produces a voltage at the output, which is proportional to the anti-logarithm of the voltage i.e., applied to the diode connected to its inverting terminal.

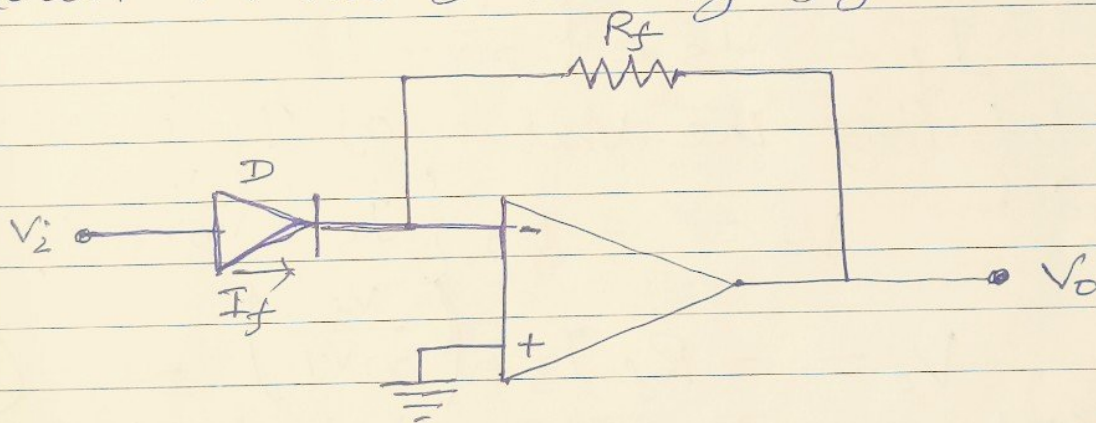The circuit diagram of an op-amp based anti-logarithmic amplifier is shown in the following figure —



In the circuit shown above, the non-inverting input terminal of the op-amp is connected to ground. It means zero

Teacher's Signature \_\_\_\_\_



Volts is applied to its non-inverting input terminal.

According to the Virtual Short Concept, the voltage at the inverting input terminal of op-amp will be equal to the voltage present at its non-inverting input terminal. So, the voltage at its inverting input terminal will be Zero Volts.

The Nodal equation at the inverting input terminal node is —

$$-I_f + \frac{0 - V_o}{R_f} = 0$$

$$\Rightarrow -\frac{V_o}{R_f} = I_f$$

$$\Rightarrow V_o = -R_f I_f \quad \text{--- (4)}$$

We know that the equation for the current flowing through a diode, when it is in forward bias, is as given below—

$$I_f = I_s e^{\left(\frac{V_f}{nV_T}\right)}$$

Substituting the value of  $I_f$  in equ<sup>n</sup> (4), we get

$$V_o = -R_f \left\{ I_s e^{\left(\frac{V_f}{nV_T}\right)} \right\}$$

$$V_o = -R_f I_s e^{\left(\frac{V_f}{nV_T}\right)} \quad \text{--- (5)}$$

The KVL equ<sup>n</sup> at the input side of the inverting terminal of the op-amp will be

$$V_i - V_f = 0$$

$$V_f = V_i$$



Substituting, the value of  $i$  in the equ<sup>n</sup> (5) we get —

$$V_o = -R_f I_s e^{\left(\frac{V_i}{mV_T}\right)}$$

Note, that, in the above equ<sup>n</sup> the parameters  $m$ ,  $V_T$  and  $I_s$  are constants. So, ~~the~~ the output voltage  $V_o$  will be proportional to the ~~anti~~ anti-natural logarithm (exponential) of the input voltage  $V_i$  for a fixed value of feedback resistance  $R_f$ .

Therefore, the op-amp based anti-logarithmic amplifier circuit discussed above will produce an output, which is proportional to the anti-natural (exponential) of the input voltage  $V_i$  when  $R_f I_s = 1V$ .

observe that the output voltage  $V_o$  is having a negative sign which indicates that there ~~exists~~ exists a  $180^\circ$  phase difference between the input and the output.

---