

B.Sc. Part II

Paper IV

Current electricity

Paper IV

Dr. Shiva Kant Mishra
Dept of Physics, H.D.J.C.
Current electricity.

Anderson Bridge :-

Anderson bridge is corrected from Maxwell bridge in which double equilibrium is found by only changing the resistance and the value of standard capacitance is constant. A variable non-inductive resistance r is connected in the detector arm and capacitor C_4 is connected between the R_4 and ends of r, C and F as shown in figure. An one end of detector D is connected on the junction point of C_4 and r and the other end is connected on B .

Let i_1, i_2, i_3 and i_4 are the combined currents in the main of arms of bridge and i_r and i_c are the current in the resistance r and capacitance C_4 .

In the position of equilibrium, there is no any current in the detector D . By Kirchhoff's 2nd law for the net ABC , BFC and CFE , we get

$$(R_1 + j\omega L) i_1 = r i_r + R_3 i_3 \quad \text{--- (1)}$$

$$R_2 i_2 = \frac{1}{j\omega C_4} i_c \quad \text{--- (2)}$$

$$r i_r + \frac{1}{j\omega C_4} i_c = R_4 i_4 \quad \text{--- (3)}$$

Again by Kirchoff's first law, for B, F and E junctions

$$i_1 = i_2 \quad \text{--- (iv)}$$


$$i_r = i_c \quad \text{--- (v)}$$

$$i_3 = i_r + i_4 = i_c + i_4 \quad \text{--- (vi)}$$

Substituting $i_1 = i_2$ and $i_r = i_c$ in equation (i) and dividing from equⁿ (ii) we have

$$\frac{(R_1 + j\omega L) i_2}{R_2 i_2} = \frac{V + R_3 i_3}{\frac{V}{j\omega C_4} - i_c}$$
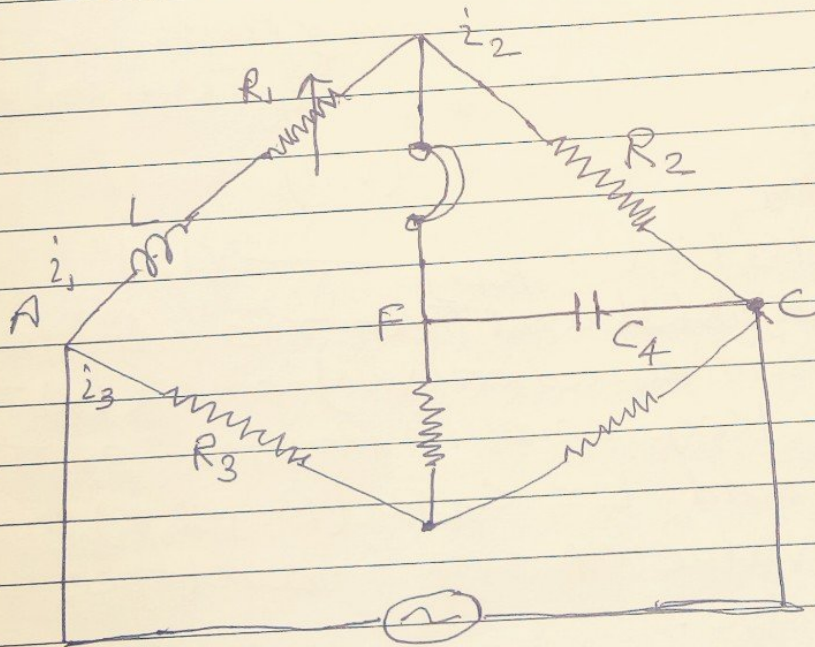
$$\text{or } \frac{R_1 + j\omega L}{R_2} = \frac{V + R_3 (i_3/i_c)}{V/j\omega C_4} \quad \text{--- (vii)}$$



Teacher's Signature _____

Substituting $i_1 = i_c$ in equation (i)
by equation (vi), we have

$$\left(r + \frac{1}{j\omega C_4} \right) i_4 = R_4 i_4 = R_4 (i_3 - i_c)$$

$$\text{or } \left(r + \frac{1}{j\omega C_4 + R_4} \right) i_4 = R_4 i_3$$

$$\text{or } \frac{i_3}{i_c} = \frac{r + \frac{1}{j\omega C_4} + R_4}{R_4}$$

whose value is substituting in equⁿ (vii),
we have

$$\frac{R_1 + j\omega L}{R_2} = \frac{r + \frac{1}{j\omega C_4 + R_4}}{R_4}$$

$$\text{or } \frac{R_1 + j\omega L}{R_2} = \frac{R_3 + j\omega C_4 (r R_4 + R_3 r + R_3 R_4)}{R_4}$$

$$\text{or } R_1 R_4 + j\omega L R_4 = R_2 R_3 + j\omega C_4 R_2 (r R_4 + R_3 r + R_3 R_4)$$

Equating separately the real & imaginary parts, we get

$$R_1 R_4 = R_2 R_3 \quad \text{and} \quad L R_4 = C_4 R_2 (r R_4 + R_3 r + R_3 R_4)$$

$$\text{or } \frac{R_1}{R_2} = \frac{R_3}{R_4} \quad \text{--- (viii)}$$

$$\text{and } L = C_4 R_2 \left[R_3 + r \left(1 + \frac{R_3}{R_4} \right) \right] \quad \text{--- (ix)}$$

First of all, R is adjusted and then r is adjusted and found the equilibrium equation (viii) and (ix) respectively.

R_3 and R_4 may keep equal in practice. In this position $R_1 = R_2$ and $L = C_4 R_2 (R_3 + 2r)$

Thus the value of self inductance is found by Anderson bridge.