

V K J U

Dr. Shiva Kant Mishra
Dept. of Physics
H. D. Jain College Ara

M. Sc. Sem III
Paper - MPHY CC-12
Electronics II
— X —

VKSU

Instrumentation Amp. using OP-Amp.




The instrumentation amp. using OP-amp. circuit is shown below. The OP-Amps 1 and 2 are non-inverting amps and OP-Amp 3 is a difference amplifier. These three OP-amps together, form an instrumentation amplifier. Instrumentation amps final output volt is the amplified difference of the input signals applied to the input terminals to OP-amp. 3, let the outputs of op-amp. 1 and op-amp. 2 be V_{o1} and V_{o2} respectively.

$$\text{Then } V_{out} = (R_3/R_2)$$

$(V_{o1} - V_{o2})$ look at

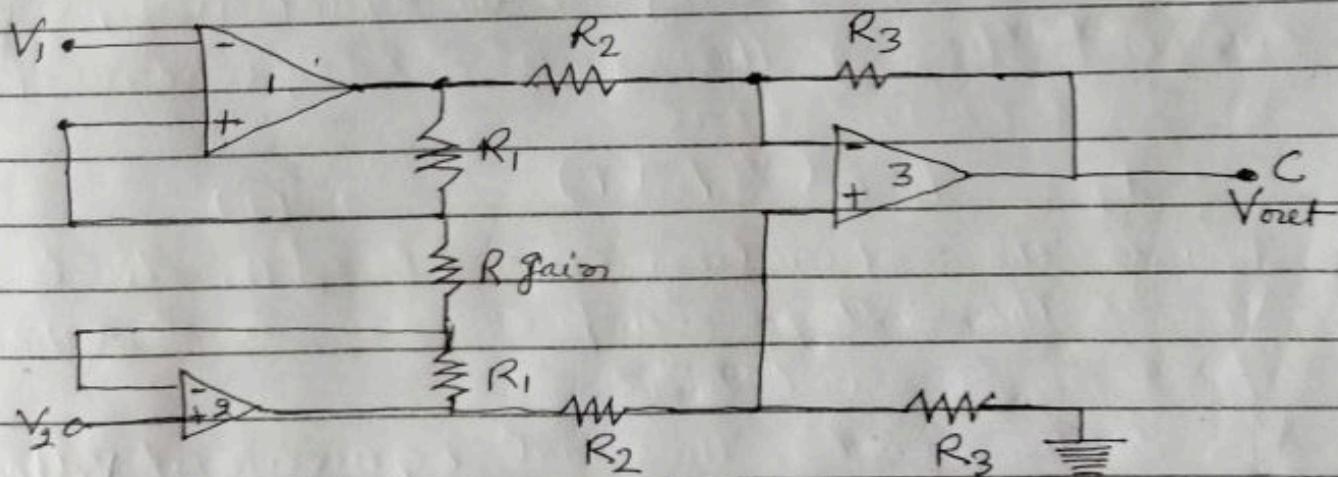The input stage of the instrumentation amp. as shown in the figure below. The instrumentation amp. derivation is discussed below.



Instrumentation Amp. using OP-amp.

fig.

VKSU



The Potential at node A is the input Voltage V_1 . Hence the Potential at node B is also V_1 , from the Virtual Short Concept. Thus, the potential at node G₁ is also V_1 .

The Potential at node D is the input voltage V_2 . Hence the Potential at node C is also V_2 , from the virtual short. Thus the Potential at node H is also V_2 .