

Dr. Shiva Kant Mishra  
Dept. of Physics  
H. D. Jain College Ara

M. Sc. Sem III  
Paper - MPHY CC-12  
Electronics II

— X —

2.

VKSU

## Logarithmic Amp. and Exponential Amp.




The electronic circuits which perform the mathematical operations such as logarithmic & exponential with an amplification are called as Logarithmic amp. and Exponential (AntiLogarithmic) Amp. respectively.
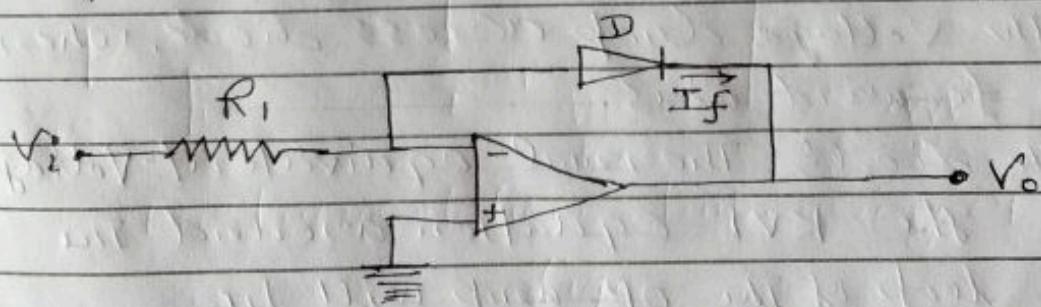
### Logarithmic Amplifier:

A logarithmic amp. or a log amp. is an electronic circuit that produces an output that is proportional to the logarithm of the applied input. This section discusses about the op-amp. based logarithmic amplifier in detail.

An op-amp. based logarithmic amp. produces a voltage at the output, which is proportional to the logarithm of the voltage applied to the resistor connected to its inverting terminal. The circuit diagram of an op-amp. based logarithmic amp. is shown in the following figure.



In the above circuit, the non-inverting input terminal of the op-amp. is connected



to ground. That means zero Volts is applied at the non-inverting input terminal of the OP-amp.

According to the virtual short concept, the voltage at the inverting input terminal of an OP-amp will be equal to the voltage at its non-inverting input terminal. So, the voltage at the inverting input terminal will be zero volts.

The nodal equation at the inverting input terminal's node is -

$$\frac{0 - V_i}{R_1} + I_f = 0$$

$$\Rightarrow I_f = V_i / R_1 \quad \text{--- (1)}$$

The following is the equation for current flowing through a diode, when it is in forward bias

$$I_f = I_s e^{(V_f / kT)} \quad \text{--- (2)}$$

- $I_s$ , is the saturation current of the diode.
- $V_f$ , is the voltage drop across diode, when it is in forward bias.
- $V_T$ , is the diode's thermal equivalent voltage.

The KVL equation around the feed back loop of the OP-amp will be

$$0 - V_f - V_o = 0$$

$$\Rightarrow V_f = - V_o$$



VKSU

Substituting the value of  $I_f$  in equation ②,  
we get  $I_f = I_s e^{(-V_o/n VT)}$  — ③

observe that the left hand side terms  
of both eqn ① and ③ are same.  
Hence, equate the right hand side term of  
those two equations as shown below —

$$\frac{V_i}{R_1} = I_s e^{(-V_o/n VT)}$$

$$\frac{V_i}{R_1 I_s} = e^{(-V_o/n VT)}$$

Applying natural logarithm on both sides,  
we get,

$$\ln\left(\frac{V_i}{R_1 I_s}\right) = -\frac{V_o}{n VT}$$

$$V_o = -n VT \ln\left(\frac{V_i}{R_1 I_s}\right)$$

Note that in the above equation, the  
parameters  $n$ ,  $VT$  and  $I_s$  are constants. So,  
the output voltage  $V_o$  will be proportional  
to the natural logarithm of the input voltage  
 $V_i$ , for a fixed value of resistance  $R_1$ .

Therefore, the OP-amp. based logarithmic amp. circuit discussed above  
will produce an output, which is proportional  
to the natural logarithm of the  
input voltage.

$V_T$  when  $R_1 T_S = I_V$ .

observed that the output voltage  $V_o$  has a - ve sign, which indicates that there exists a  $180^\circ$  phase difference between the input and the output.

Logarithmic Amplifiers :-