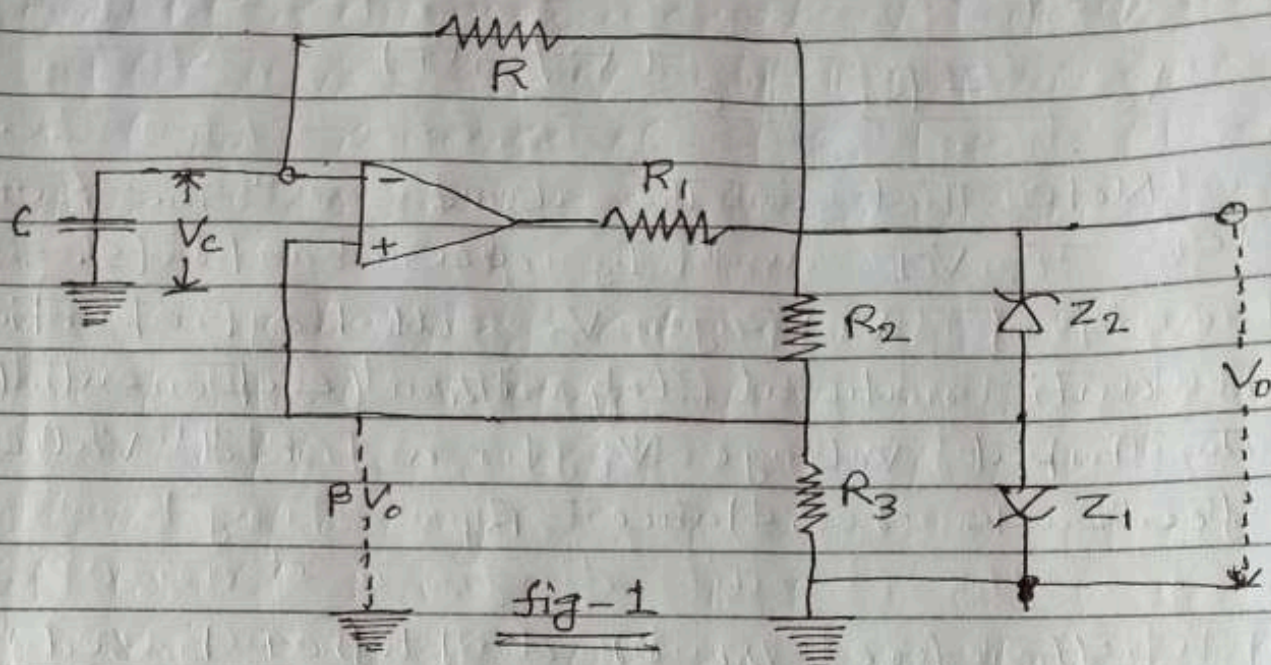


## 47 VKSU Astable Multivibrator

The operational amplifier operating as free running (astable) Multivibrator is shown in figure - 1




Astable Multivibrator

In free running multivibrator, there are two states which remain momentarily stable and the circuit switches repeatedly between these two states. OP-amplifier enjoys both +ve and -ve feedbacks and ~~has~~ has a timing capacitor C, at its inverting input terminal.

The output voltage  $V_0$  is limited by the breakdown voltage  $+V_{0s}$  and  $-V_{0s}$  of the two Zener diodes  $Z_1$  and  $Z_2$  connected back to back across the output terminals of the

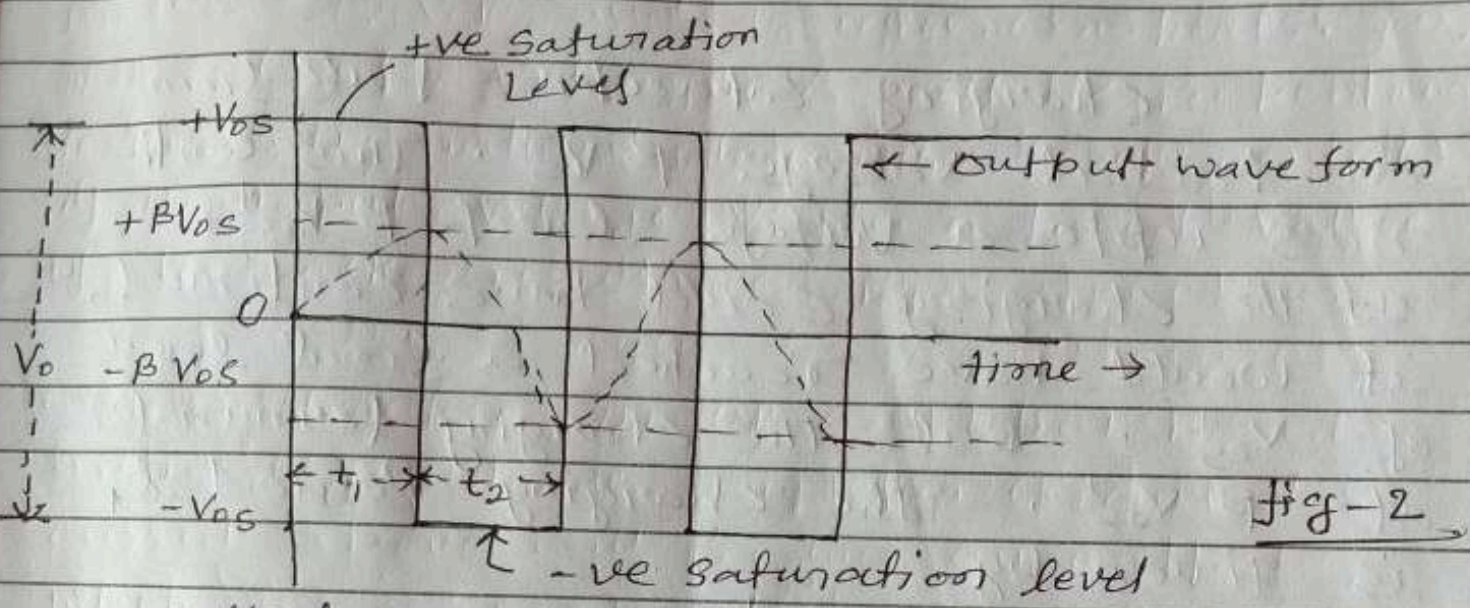OP-amplifier. Thus  $V_o$  will be either  $+V_{os}$  (or  $V_{os}^+$ ) or  $-V_{os}$  ( $V_{os}^-$ ). A fraction  $\beta = R_3 / (R_2 + R_3)$  of  $V_o$  is fed back to the non-inverting input. Thus in one state the amplifier output ~~reaches~~ reaches a +ve saturation level ( $V_o = +V_{os}$ , diode  $Z_1$ ) The output waveform in this a square wave figure (2)



output waveform of free running multivibrator

The input voltage  $V_{in}$  to the amplifier is

$$V_{in} = V_c - \beta V_o$$

When  $V_{in} < 0$ , or  $V_c < \beta V_o = \beta V_{os}^+$

Capacitor  $C$  charges exponentially towards  $V_{os}^+$  through a time constant  $RC$ . The output  $V_o$ , remains constant at  $V_{os}^+$  until  $V_c = \beta V_{os}^+$ . So, that  $V_{in} = V_c - \beta V_{os}^+ = 0$ , i.e. The potential difference between the two input terminals approaches zero, and the amplifier output

reverses to  $V_{os}$ . Now  $C$  charges exponentially towards  $V_{os}$ .

Then  $V_i = V_c - \beta V_o = V_c + \beta V_{os}^+$ . The output remains constant at  $V_{os}^-$

until  $V_c = -\beta V_{os}^-$  at which  $V_i = 0$  and the reverse of state takes place.

These waveforms are shown in fig-2.

Charging capacitor starts from an initial voltage  $\beta V_{os}^-$ . This continues upto a voltage level  $\beta V_{os}^+$ .

If the charging could have continued, it would have reached a final level of  $V_{os}^+$ . But the charging terminates at  $\beta V_{os}^+$ . The charging period  $t_1$  is given by

$$t_1 = RC \log_e \frac{V_{os}^+ - \beta V_{os}^-}{V_{os}^+ - \beta V_{os}^+}$$

$$= RC \log_e \frac{V_{os}^+ - \beta V_{os}^-}{V_{os}^+ (1 - \beta)}$$

The 2nd charging time from  $\beta V_{os}^+$  to  $-\beta V_{os}^-$  will be

$$t_2 = RC \log_e \frac{V_{os}^- - \beta V_{os}^+}{V_{os}^- (1 - \beta)}$$

If  $V_{os}^+ = V$  and  $V_{os}^- = -V$  Then  $t_1 = t_2$  So that we shall have period

VKSU

of one oscillation or time period as

$$T = t_1 + t_2$$

$$= RC \log_e \frac{V + \beta V}{V(1 - \beta)} + RC \log_e \frac{-V - \beta V}{-V(1 - \beta)}$$

$$= RC \log_e \frac{(1 + \beta)}{(1 - \beta)} + RC \log_e \frac{(1 + \beta)}{(1 - \beta)}$$

$$= 2 RC \log_e \frac{(1 + \beta)}{(1 - \beta)} \quad \text{--- (1)}$$

$$= 2 RC \log_e \frac{1 + R_3 / (R_2 + R_3)}{1 - R_3 / (R_2 + R_3)}$$

$$= 2 RC \log_e \left[ 1 + \frac{2R_3}{R_2} \right]$$

If  $\beta$  is chosen to be 0.473 then  $T = 2RC$ ,  
so that frequency of oscillation is

$$f = \frac{1}{T} = \frac{1}{2RC}$$

From equ<sup>n</sup> (1), we observe that time period is independent of saturation level  $V_{os}^+$  and  $V_{os}^-$  and depends only on time constant  $RC$  and feedback factor  $\beta$ .

Astable multivibrator is very useful for fixed frequency applications in audio frequency range (10 Hz - 10 KHz), At frequencies greater than 10 KHz, The delay time of the amplifier for going from one

VKSN



State of saturation to another state of saturation becomes significant further, slow rate of OP-amplifier also sets a limit on the ~~rise~~ rise and fall times of square wave output waveform.