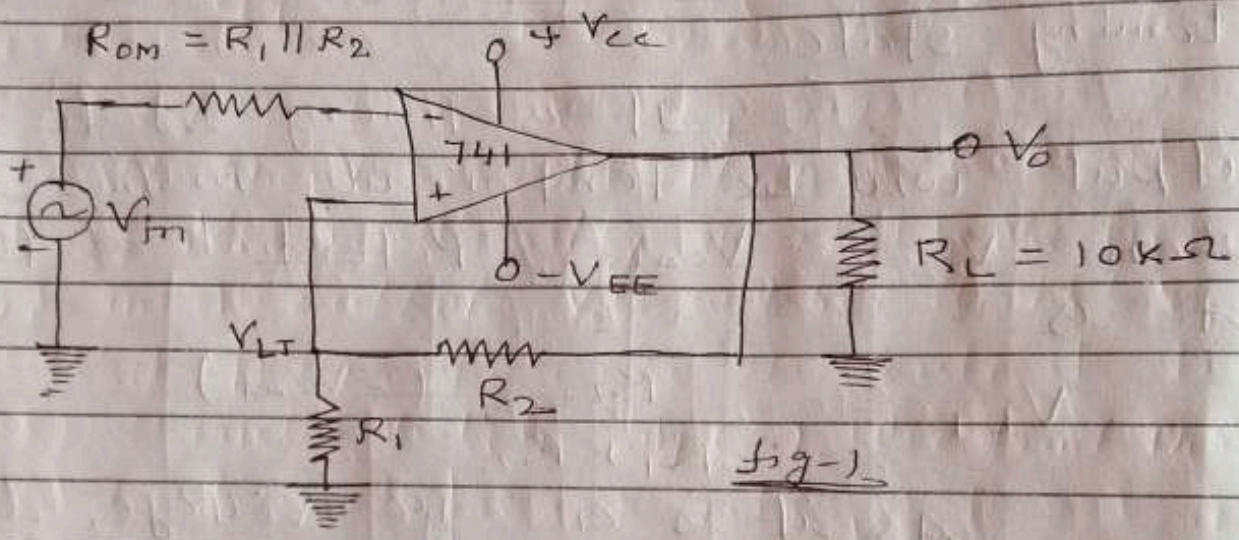




6.) VKSU Schmitt trigger

From fig (1), it is an inverting comparator with positive feedback and is capable of converting any irregular shaped input into a square wave output fig (2).



Schmitt trigger, inverting comparator with positive feedback.

There will be two voltage levels - one will be called the upper threshold voltage, V_{UT} and the other as lower threshold voltage, V_{LT} . Every time the input voltage, V_m , will exceed these voltage levels, the output V_o will change the state and attain $\pm V_{sat}$ value. These threshold voltages are obtained by using a potential divider $R_1 - R_2$ network fig (1). The voltage across R_1 is feedback to the non-inverting input.

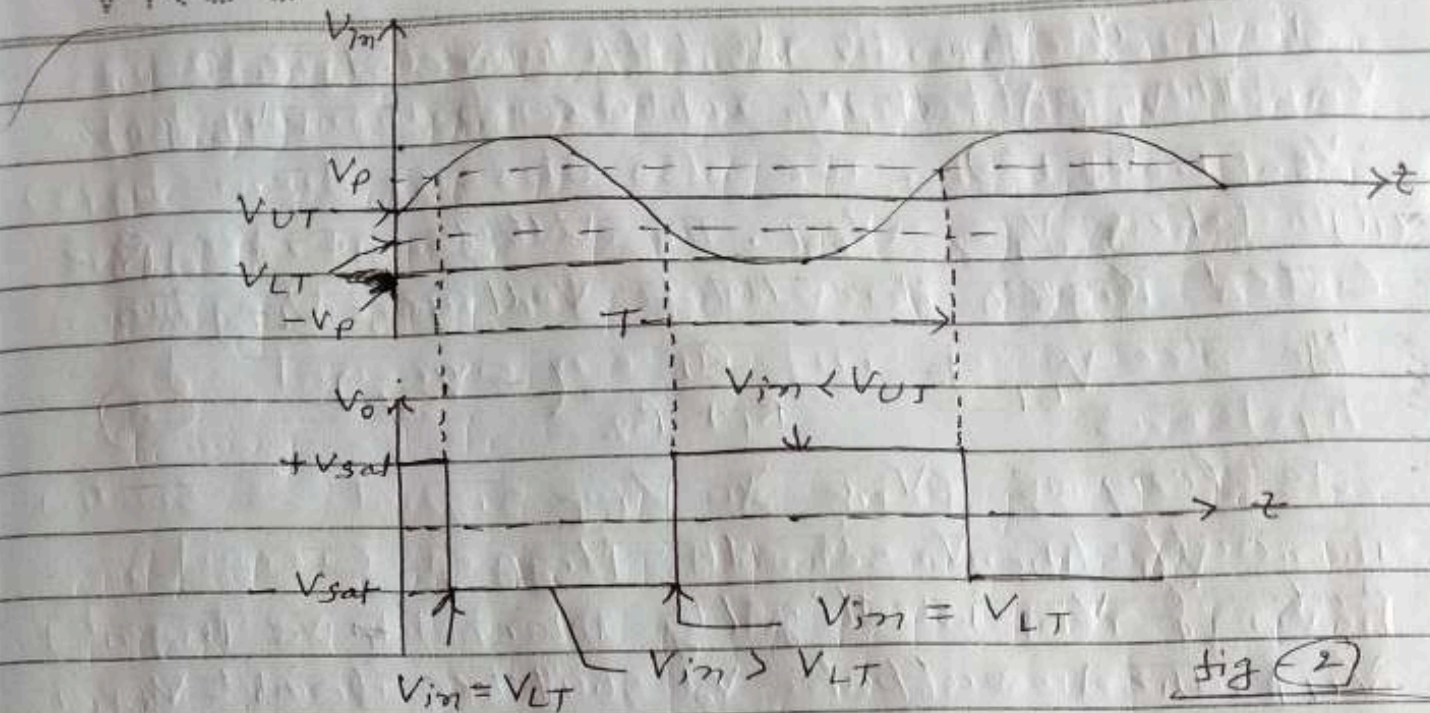


fig (2)

Input output wave forms. Note that if $R_1 = 100 \text{ ohm}$, $R_2 = 56 \text{ K ohm}$ and $V_{in} = 1 \text{ Volt}$ PP then $V_p = 0.5 \text{ Volt}$, $V_{UT} = 25 \text{ mV}$ & $V_{LT} = 25 \text{ mV}$.

The voltage across R_1 , which is fed back to the non-inverting terminal is a variable reference ~~the~~ threshold voltage that depends on the value and polarity of the output voltage V_o .

(i) When $V_o = +V_{sat}$, the voltage across R_1 is called upper threshold voltage, V_{UT} , given by

$$V_{UT} = \frac{R_1}{R_1 + R_2} (+V_{sat}) \quad \text{--- (1)}$$

As long as $V_{in} < V_{UT}$,
output V_o is at $+V_{sat}$



VKSU

But if V_{in} is slightly more +ve than V_{UT} Then output, V_o switches from $+V_{sat}$ to $-V_{sat}$, fig (2)

(ii) when $V_o = -V_{sat}$ The voltage across R_1 is called lower threshold voltage, V_{LT} , given

by
$$V_{LT} = \frac{R_1}{R_1 + R_2} (-V_{sat})$$
 (2)


As long as $V_{in} > V_{LT}$ }
 output V_o is at $-V_{sat}$ }

But if V_{in} is slightly more +ve than V_{LT} Then output V_o switches from $-V_{sat}$ to $+V_{sat}$ [fig-2]

Thus as indicated in fig (2), we find that

⇒ at $V_{in} = V_{UT}$, when input voltage V_{in} is increasing, output voltage V_o switches to $-V_{sat}$.

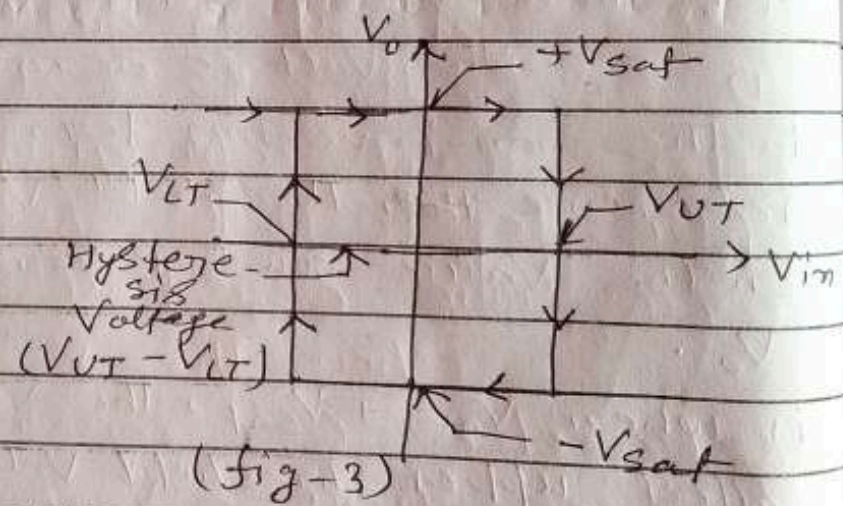⇒ at $V_{in} = V_{LT}$, when input voltage V_{in} is decreasing, output voltage V_o switches to $+V_{sat}$



(fig-3)
 V_o vs V_{in} Plot of the hysteresis voltage

— (3)

Whenever any circuit changes from one state to a 2nd state at some input signal



and then reverts from the second to the first state at a different input signal, the circuit is said to exhibit hysteresis.

There exists a hysteresis zone or a dead band condition fig(3). When input of comparator exceeds V_{UT} , the output switches from $+V_{sat}$ to $-V_{sat}$ and then reverts back to original state, $+V_{sat}$, when input goes below V_{LT} . The hysteresis voltage is equal to the difference between V_{UT} and V_{LT} .

i.e.

$$V_H = V_{UT} - V_{LT}$$

$$= \frac{R_1}{R_1 + R_2} [+V_{sat} - (-V_{sat})]$$

For OP-Amp 741, $+V_{sat} = 14$ Volt, $-V_{sat} = -14$ Volt. if $R_1 = 100 \Omega$ and $R_2 = 56 K \Omega$ with $V_{in} = 1$ volt peak to peak sine wave in fig(1), then

$$V_{UT} = \frac{100}{56100} (14) = 25 \text{ mV}$$

$$V_{LT} = \frac{100}{56100} (-14) = -25 \text{ mV}$$

So that hysteresis voltage will be

$$V_H = V_{UT} - (-V_{LT})$$

$$= 25 - (-25) = 50 \text{ mV}$$



VKSU

So the different Threshold Voltages (V_{UT} and V_{LT}) at the input result in hysteresis or backlash. We also observe from fig (3) that $V_{UT} > V_{LT}$. i.e. Circuit triggers at a higher ~~to~~ Voltage for increasing than for decreasing inputs on account of hysteresis.

If peak to peak signal is smaller than V_H then Schmitt trigger circuit, having responded at a Threshold Voltage by a transition in one direction, would never reset itself, i.e. once the output has jumped to $+V_{sat}$, it would remain at this level and never returns to $-V_{sat}$.