

K30
Dr. Shiva Kant Mishra
Dept. of Physics
H. D. Jain College Ara

M. Sc. Sem III
Paper - MPHY CC-12
Electronics II

————— X —————



Circuit with truth table is shown in fig.

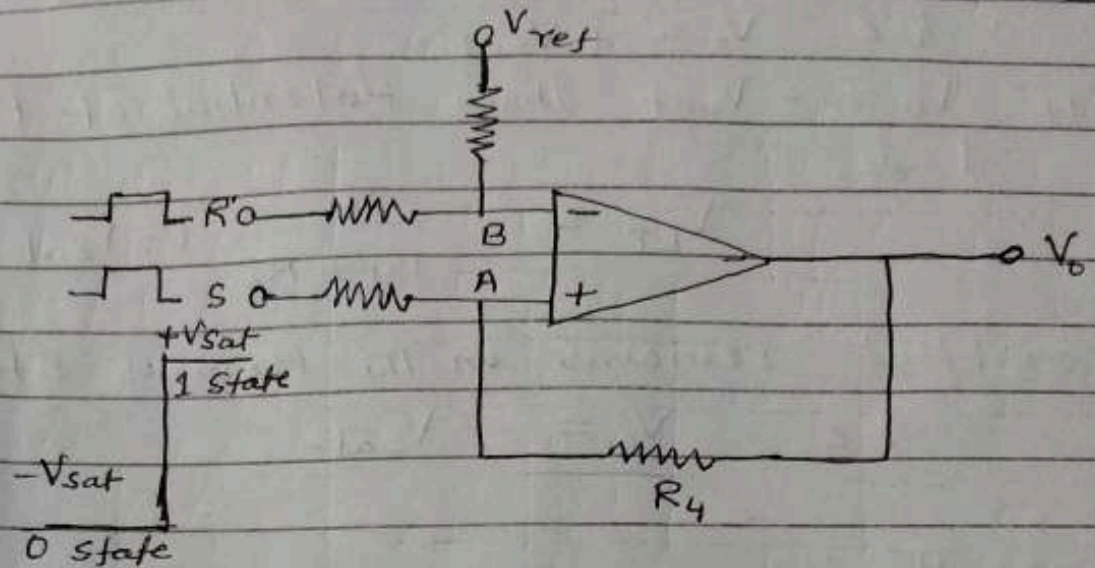


fig $V_0 = +V_{sat}, V_0 = -V_{sat}$
S-R flip flop, S is set, R is reset

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	not used

Case 1 :- $S=0, R=0$, i.e. no pulse is applied at S and R inputs. Taking

$$V_{ref} = 0.$$

If $V_0 = +V_{sat}$ then potential at point A is

$$V_{UT} = \frac{R_1}{R_1 + R_4} (+V_{sat})$$

VKSU

output remains in the previous state

i.e. $V_o = +V_{sat}$

If $V_o = -V_{sat}$ then potential at point A is,

$$V_{LT} = \frac{R_1}{R_1 + R_4} (-V_{sat})$$

output remains in the previous state

i.e. $V_o = -V_{sat}$

Case II :

$$S = 0, R = 1$$

If $V_o = +V_{sat}$

Potential at point A is

$$V_{UT} = \frac{R_1}{R_1 + R_4} (+V_{sat})$$

Now at R terminal a pulse is given of magnitude at point B to be ~~generally~~ greater than V_{UT} . Then output is

$$V_o = -V_{sat}$$

If $V_o = -V_{sat}$

Potential at point A is

$$= \frac{R_1}{R_1 + R_4} (-V_{sat})$$

If a pulse is given to R-terminal then output $V_o = -V_{sat}$

VKSU

i.e. with $S=0$ and $R=1$ output is at Reset state, i.e. 0 state ($-V_{sat}$).

Case - III -

When $S=1$, $R=0$

If $V_o = +V_{sat}$

Potential at Point A is

$$= \frac{R_1}{R_1 + R_4} (+V_{sat}) + \text{Pulse}$$

If a Pulse is given to S terminal, Potential at Point A is more positive and hence output

$$V_o = +V_{sat}$$

If $V_o = -V_{sat}$

Potential at Point A is

$$= \frac{R_1}{R_1 + R_4} (-V_{sat}) + \text{Pulse}$$

If the amplitude of the Pulse is more than the -ve Potential at Point A due to $V_o = -V_{sat}$ then resultant Potential at Point A is positive i.e. $V_o = +V_{sat}$. That is with $S=1$ and $R=0$ it is in set state (1 state or $+V_{sat}$)

Case - IV

$S=1$, $R=1$, not used.