

Dr. Annu Kumari
Dept. of Physics

H. D. Sain college, Agra

PG III

Paper / Unit - CC 12 / II

Topic - used of 555 IC Timer

(A) Timer as Monostable Multivibrator

fig (2) is to be triggered externally
 $+V_{cc} (+5V)$

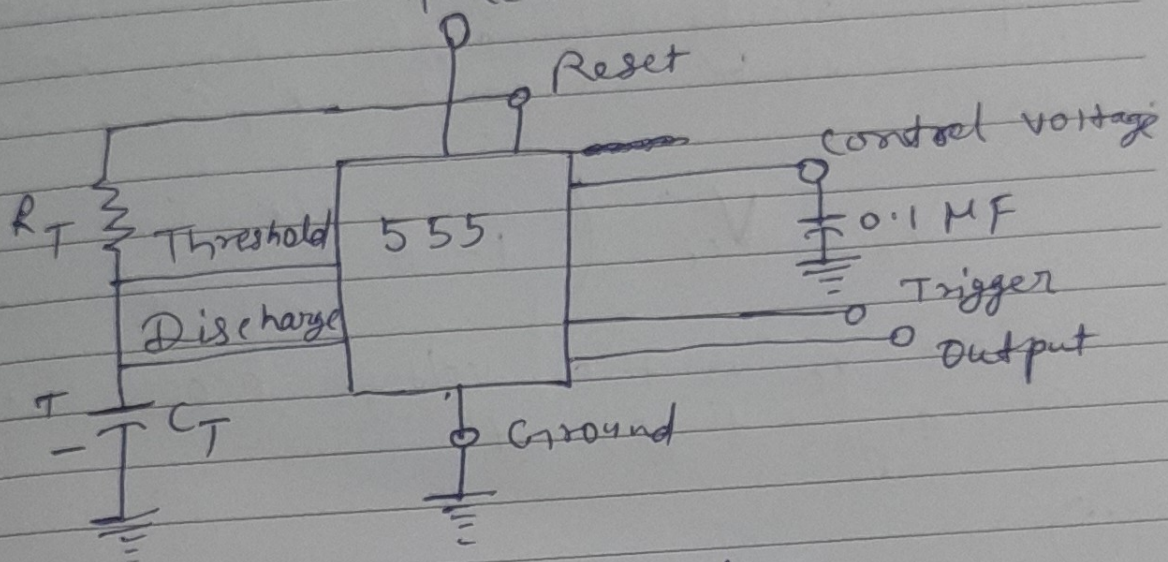


fig (2) 555 timer

for monostable mode of operation.
 We note that:

(i) When no trigger input is applied, capacitor C_T is held in the discharged state. In this state output is low.

(ii) When trigger input is applied and as the trigger voltage passes through $V_{cc}/3$ (threshold level of comp. - 2), comparator - 2 changes

its output state so that flip flop is set i.e. $\bar{Q} = 0$ and transistor Q_1 becomes OFF. ~~the~~ therefore timing cycle begins i.e. capacitor C charges up exponentially through R_T towards V_{CC} with time constant $R_T C_T$ according to

$$V_c = V_{CC} \left(1 - e^{-t/R_T C_T} \right) \quad \text{--- (i)}$$

where V_c is the voltage across the capacitor at any time, t .

(iii) when this voltage V_c , reaches $2V_{CC}/3$ (threshold level of comparator-1), as

it is connected to threshold terminal, comparator-1 changes its output state so that flip flop is reset i.e.

$\bar{Q} = 1$. This makes the transistor Q_1

ON and the capacitor discharges rapidly to ground; the timing cycle is ~~combined~~ completed. Once the circuit is triggered, it is insensitive to further triggering pulses until the timing cycle is completed.

DATE / /

(iv) from points (ii) and (iii), we note that time period of the timing cycle is the time required for the capacitor to charge from zero to $2V_{CC}/3$. This period can be obtained on putting $V_c = 2V_{CC}/3$ at $t = T$ in eqn (1). That is

$$2V_{CC}/3 = V_{CC} \left(1 - e^{-T/R_T C_T} \right)$$

$$\text{or } T = R_T C_T \log_e \frac{V_{CC}}{V_{CC} - \frac{2}{3}V_{CC}}$$

$$\cong 1.1 R_T C_T \quad \text{--- (2)}$$

This pulse width is determined by external resistance & capacitance.

DATE / /

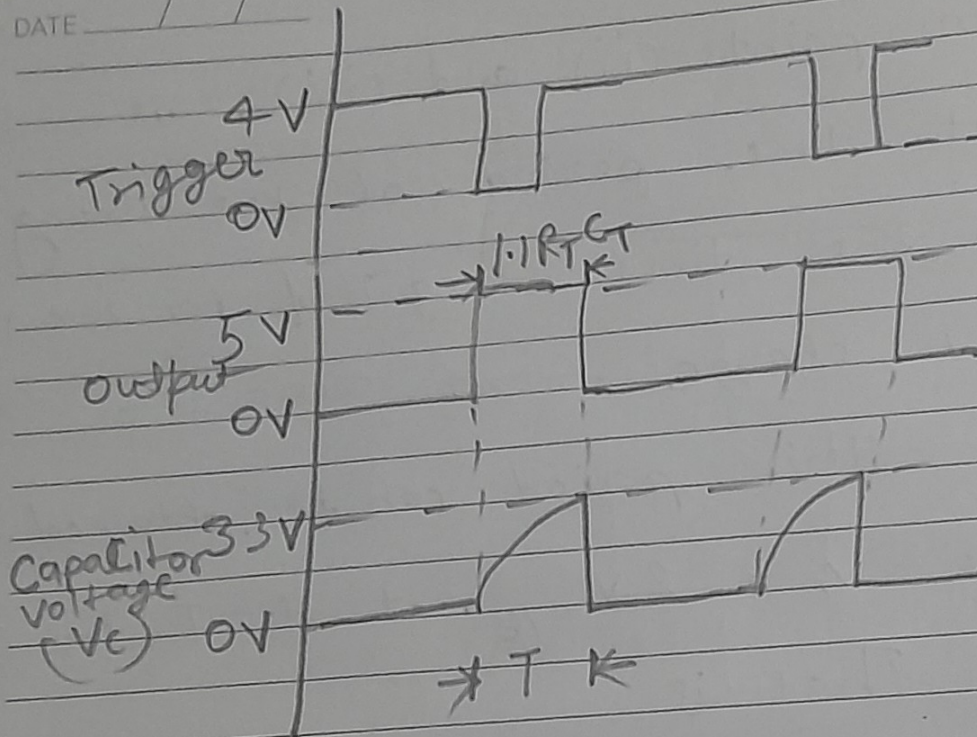


fig (3) 555 timer used as a one shot multivibrator.

NOTE $V_c = 2 \frac{V_{cc}}{3} = 2 \times \frac{5}{3} = 3.3V$

(B) Timer used as Astable multivibrator

External connections for astable operation are shown in fig (4). In this operation, circuit does not require any external trigger signal; therefore, trigger terminal is connected to threshold terminal so that at all time, V_c is applied to both these inputs. Further two series resistors R_A and R_B are also used, whose common junction is connected

to discharge terminal. Its operation is as follows:

operation :-

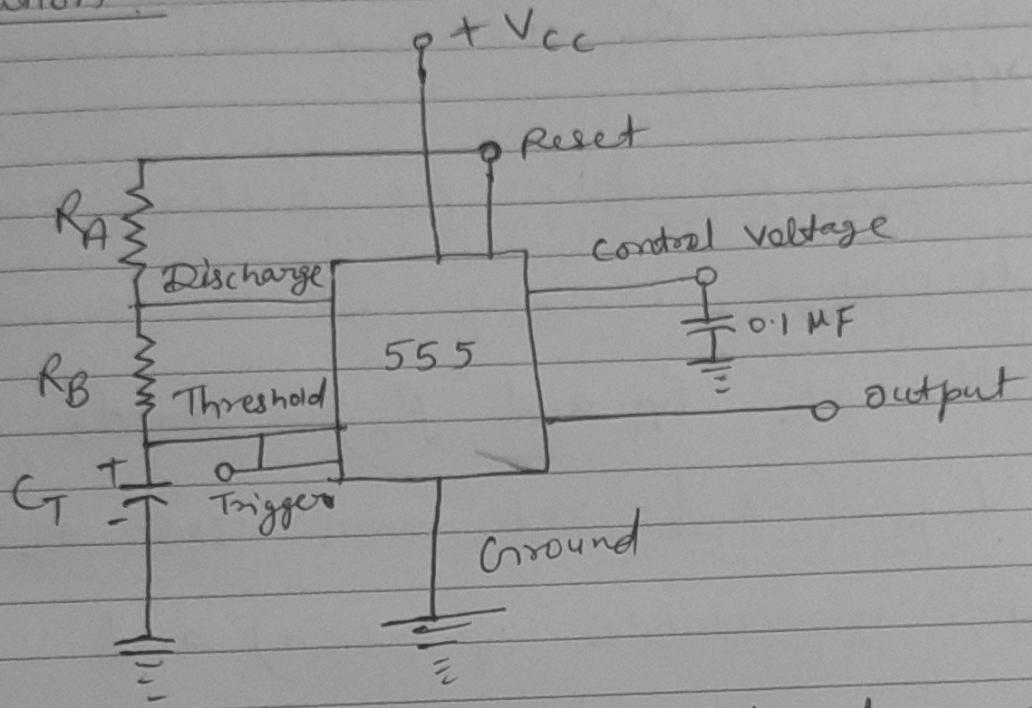


fig (4) 555 timer: External connections for astable operation.

During charging up period transistor Q_1 is held open by flip flop and capacitor charges through series connected resistors R_A and R_B . When voltage across capacitor reaches $\frac{2V_{cc}}{3}$ (reference level of comparator - 1) comparator - 1 changes its output state and it changes the state of flip flop so that transistor Q_1 is now ON. The capacitor then discharges through R_B until its

DATE: / /

voltage drops to $V_{CC}/3$ (reference level of comparator 2). This comparator then changes the state of flip flop again which in turn makes the transistor Q_1 OFF and thus the cycle repeats itself.

Charging period: - As is clear from above description, charging of the capacitor (through R_A and R_B) starts from $V_{CC}/3$ (and not from zero as in case of monostable operation) and continues upto $2V_{CC}/3$.

Therefore eqn (2) for this case becomes:

Charging period:

$$\begin{aligned} T_1 &= C(R_A + R_B) \log_e \frac{V_{CC} - V_{CC}/3}{V_{CC} - 2V_{CC}/3} \\ &= C(R_A + R_B) \log_e 2 \\ &= 0.7 (R_A + R_B) C \end{aligned}$$

Discharge period : - Capacitor discharges (through R_B only) from $2V_{CC}/3$ towards zero volt. This discharge is terminated at $V_{CC}/3$ at which comparator-2 changes state. Hence discharge period is determined by the

Eqnⁿ

$$T_2 = C R_B \log_e \frac{0 - 2V_{CC}/3}{0 - V_{CC}/3}$$

$$= 0.7 R_B C.$$

Total period : $T = T_1 + T_2$

$$= 0.7 (R_A + 2R_B) C$$

charging and discharging

intervals differ by $0.7 R_A C$.