

## Assignment 1

- 1) Explain operating point of BJT.
- 2) What is fixed biased circuit?
- 3) What do you mean by emitter stabilized biased circuit?  
Explain.
- 4) Explain voltage divider circuit in detail.