

Flip Flops

{Latch (NOR and NAND) }

Presented By:

Suraj Prakash

Asst. Professor

Outline

- S-R Latch
- NOR
- NAND

S- R Latch

SR Flip-Flop



The **SR flip-flop**, also known as a *SR Latch*, can be considered as one of the most basic sequential logic circuit possible. This simple flip-flop is basically a one-bit memory *bistable* device.

It has two inputs S and R and two outputs Q and Q'. The state of this latch is determined by the condition of Q. **If Q is 1 the latch is said to be SET** and **if Q is 0 the latch is said to be RESET**. Then the SR description stands for “Set-Reset”. This SR Latch or Flip flop can be designed either by two cross-coupled NAND gates or two-cross coupled NOR gates.


When we design this latch by using NOR gates, it will be an **active high S-R latch**. That means it is SET when $S = 1$.

When we design this latch by using NAND gates, it will be an **active low S-R latch**. That means it is SET when $S = 0$. SR Flip Flop is also called SET RESET Flip Flop.

NOR Gate S R Latch

 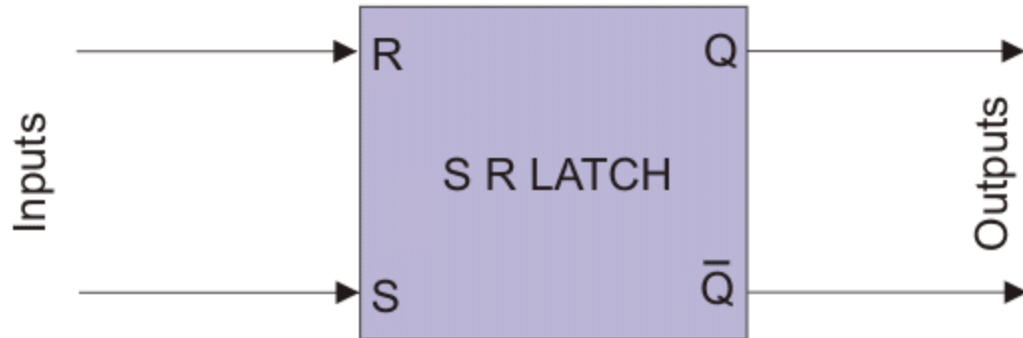

Working of NOR Gate S R Latch

 

In the above logic circuit if $S = 1$ and $R = 0$, Q becomes 1.


NOR gate always gives output 0 when at least one of the inputs is 1.

So when S is applied as 1 the output of gate $G2$ i.e. Q' is 0 irrespective of the condition of second input Q to the gate.

Now Q' is the input of gate $G1$ so both the inputs of $G1$ become 0 as R is already 0. So, the output of $G1$ is now 1.

So whatever may be the previous condition of Q , it always becomes $Q = 1$ and $Q' = 0$ when $S = 1$ and $R = 0$. This is called the SET condition of the latch.

Working of NOR Gate S R Latch

 


In the above logic circuit if $S = 0$ and $R = 1$, Q becomes 0.

As we already said, a NOR gate always gives output 0 when at least one of the inputs is 1.

So when R is applied as 1, the output of gate $G1$ i.e. Q is 0 irrespective of the condition of the second input Q' to the gate.

So, whatever may be the previous condition of Q , it always becomes 0 this 0 is then fed back to the input of gate $G2$. As here S is already 0, both inputs of $G2$ are 0. Hence the output of $G2$ i.e. Q' will be 1. So, $Q = 0$ and $Q' = 1$ when, $S = 0$ and $R = 1$. This is called the RESET condition of the latch.

Working of NOR Gate S R Latch

 

In the above logic circuit if $S = 0$ and also $R = 0$, Q remains the same as it was.

First suppose Q is previously 1.

Now the inputs of $G2$ are 0 and 1 as $S=0$ and $Q=1$. So output of $G2$ i.e. Q' is 0.

Now both inputs of $G1$ are 0 as $R=0$ and $Q'=0$. So the output of $G1$ i.e. Q is 1.


Now suppose Q is previously 0.

Now both inputs of $G2$ are 0 and 1 as $S = 0$ and $Q = 0$. So the output of $G2$ i.e. Q' is 1.

Now the inputs of $G1$ are 0 and 1 as $R=0$ and $Q' = 1$. So the output of $G1$ i.e. Q is 0.

So it is proved that Q remains the same as it is when $S = 0$ and also $R = 0$ in SR latch.

Working of NOR Gate S R Latch

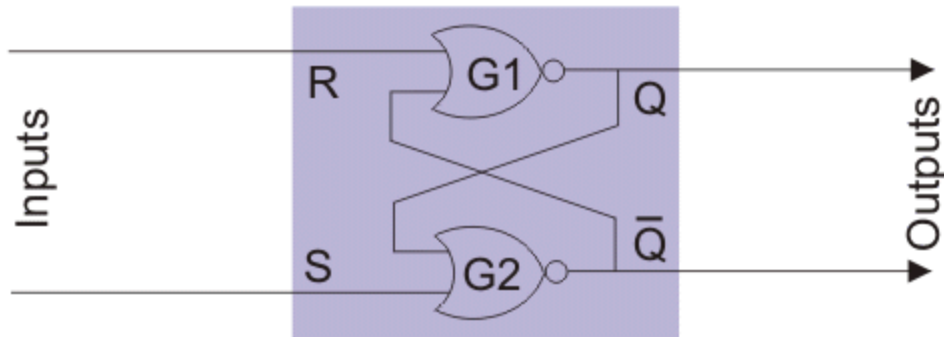

In the above logic circuit if $S = 1$ and also $R = 1$, the condition of Q is totally unpredictable.

First suppose Q is previously 1.

Now both inputs of $G2$ are 1 as $S = 1$ and $Q = 1$. So output of $G2$ i.e. Q' is 0.

Now the inputs of $G1$ are 1 and 0 as $R = 1$ and $Q' = 0$. So the output of $G1$ i.e. Q is 0. That means Q is changed.

Now Q is 0. So inputs of $G2$ are 1 and 0 as $S = 1$ and $Q = 0$. So the output of $G2$ i.e. Q' is 0. That means Q' is unchanged. Now the inputs of $G1$ are 1 and 0 as $R = 1$ and $Q' = 0$. So the output of $G1$ i.e. Q is 0. That means Q is unchanged.

So, when both S and R are 1, it becomes unpredictable whether the value of output Q will be changed or unchanged. This condition of SR latch normally avoided.


Truth Table of S R Latch

Q is previously state and Q+1 is current state.

S	R	Q	Q ₊₁	STATE
0 0	0 0	0 1	0 1	NC
0 0	1 1	0 1	0 0	RESET
1 1	0 0	0 1	1 1	SET
1 1	1 1	0 1	X X	INVALID

There is another type of latch which is SET when, $S = 0$ (LOW), and this latch is known as Active Low SR Latch (NAND S R Latch).

NAND Gate S R Latch

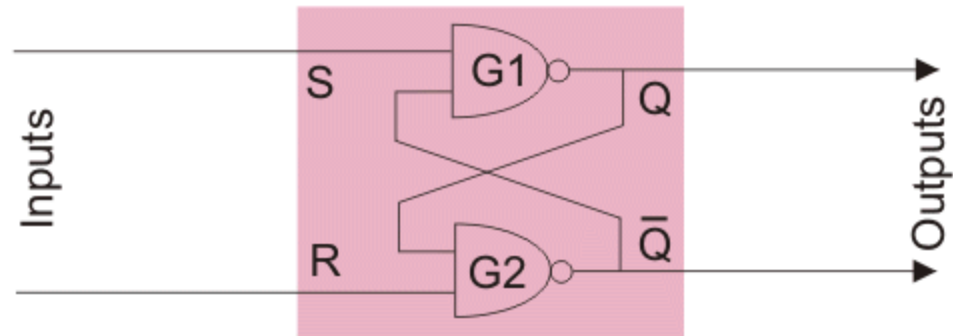

S	R	Q	Q ₊₁	STATE
0 0	0 0	0 1	X X	INVALID
0 0	1 1	0 1	1 1	SET
1 1	0 0	0 1	0 0	RESET
1 1	1 1	0 1	0 1	NC